
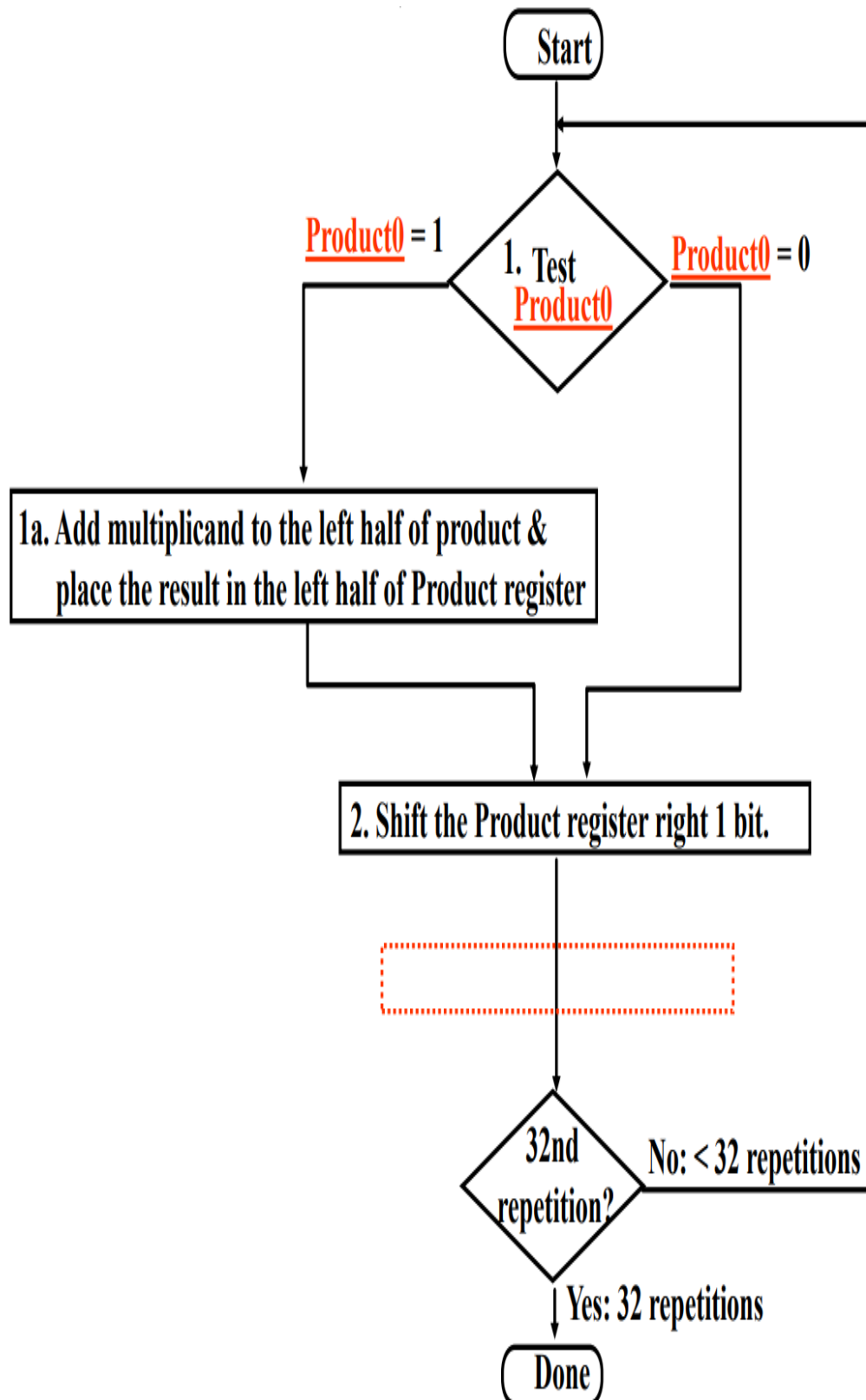


Assignment 3 Report


ASM

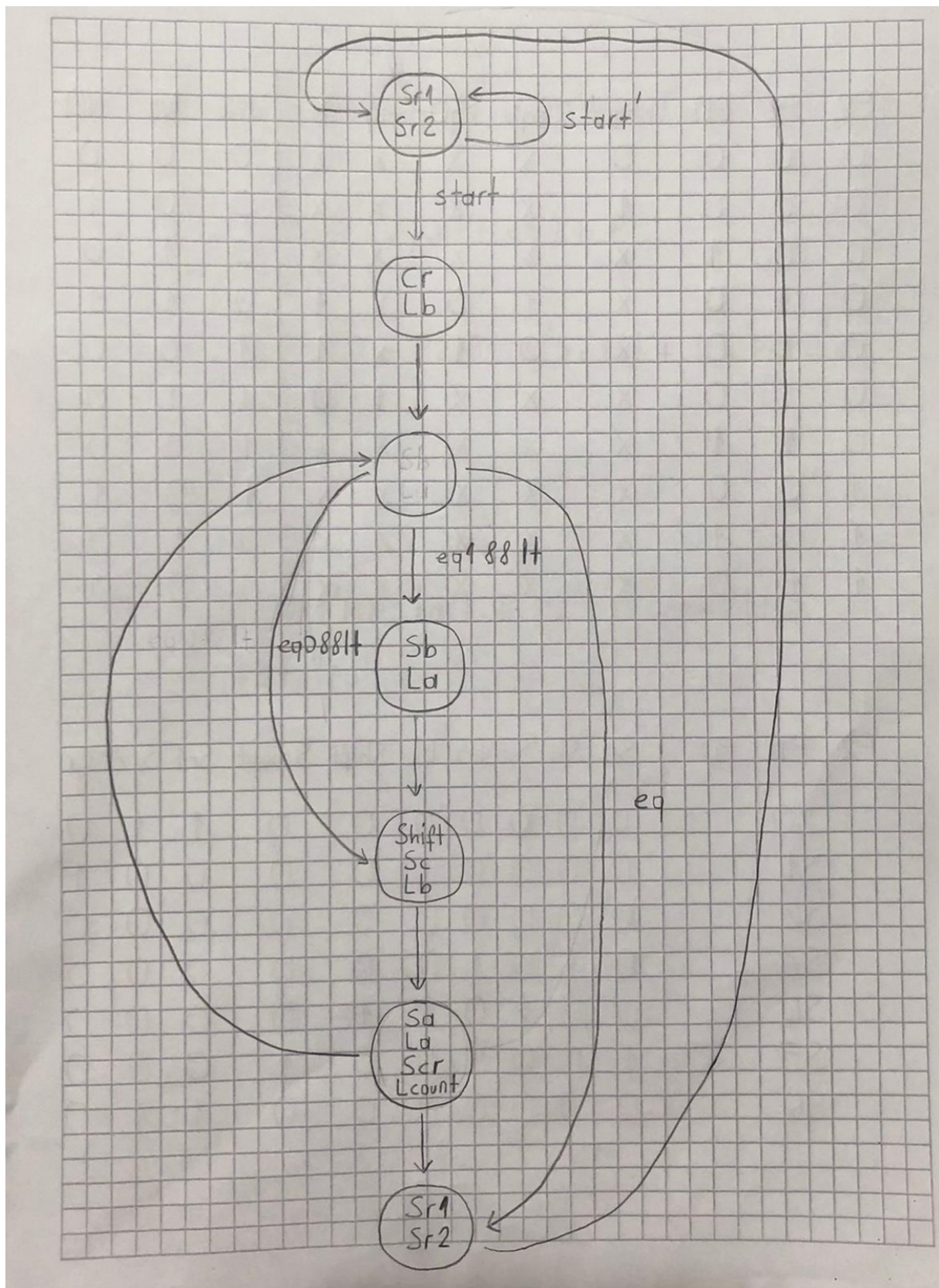

State Diagram



Datapath

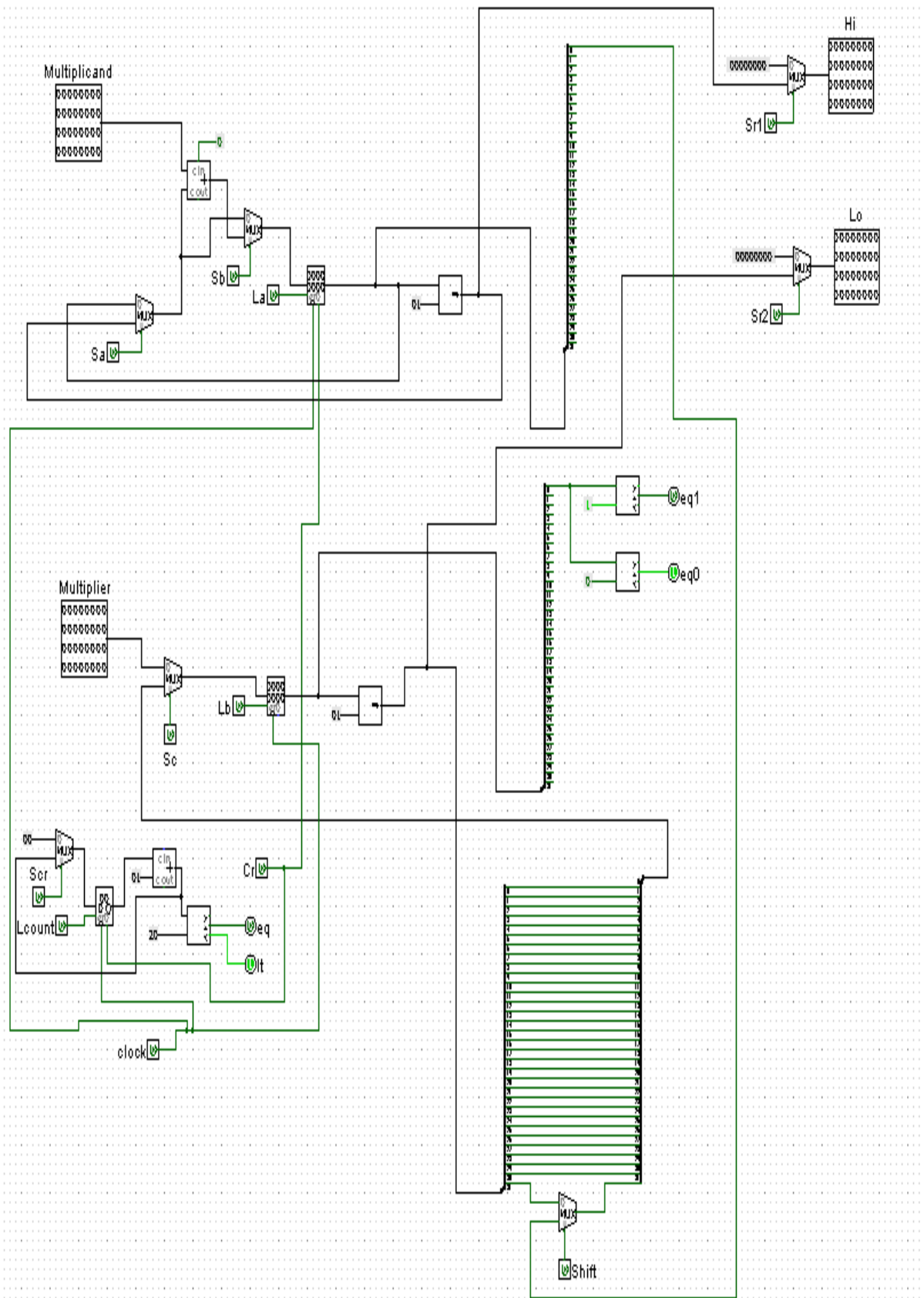

Datapath Input

1-Sa: This signal provides that we can take a current most significant 32 bit of product.

2-Sb: This signal provides that we can add multiplicand to most significant bit of product.

3-Sc: This signal provides that we can take a current less significant 32 bit of product.

4-La: This signal provides that we can load current most significant 32 bit of product to register.

5-Lb: This signal provides that we can load current less significant 32 bit of product to register.

6-Shift: This signal provides that we can shift 0th bit of most significant 32 bit product to 31th bit of less significant 32 bit product.

7- Scr: This signal provides that we can take a current counter register value.

8-Lcount: This signal provides that we can load current counter value to register.

9-Sr1: This signal provides that we can show the most significant 32 bit of result on Hi pin.

10-Sr2: This signal provides that we can show the less significant 32 bit of result on Lo pin.

11-Cr: This signal provides that we can clean the content of most significant 32 bit of product register and counter register.

12-Clock

Datapath Output

1-eq1: This signal decides that 0th bit of most significant 32 bit of product is equal to 1 or not.

2-eq0: This signal decides that 0th bit of most significant 32 bit of product is equal to 0 or not.

3-eq: This signal decides that counter register value is equal to 32 or not.

4-lt: This signal decides that counter register value is less than 32 or not.

Control Unit

Truth Tables

P2	P1	P0	start	eq1	eq0	eq	lt	N2	N1	N0
0	0	0	0	-	-	-	-	0	0	0
0	0	0	1	-	-	-	-	0	0	1
0	0	1	-	-	-	-	-	0	1	0
0	1	0	-	1	0	0	1	0	1	1
0	1	0	-	0	1	0	1	1	0	0
0	1	0	-	-	-	1	0	1	1	0
0	1	1	-	-	-	-	-	1	0	0
1	0	0	-	-	-	-	-	1	0	1
1	0	1	-	-	-	-	-	0	1	0
1	1	0	-	-	-	-	-	0	0	0


P2	P1	P0	Sa	Sb	Sc	La	Lb	Shift	Scr	Lcount	Sr1	Sr2	Cr
0	0	0	0	0	0	0	0	0	0	0	1	1	0
0	0	1	0	0	0	0	1	0	0	0	0	0	1
0	1	0	0	0	0	0	0	0	0	0	0	0	0
0	1	1	0	1	0	1	0	0	0	0	0	0	0
1	0	0	0	0	1	0	1	1	0	0	0	0	0
1	0	1	1	0	0	1	0	0	1	1	0	0	0
1	1	0	0	0	0	0	0	0	0	0	1	1	0

Boolean Expressions

$$N2 = P2'P1P0'eq0lt + P2'P1P0'eq + P2'P1P0 + P2P1'P0'$$

$$N1 = P2'P1'P0 + P2'P1P0'eq1lt + P2'P1P0'eq + P2P1'P0$$
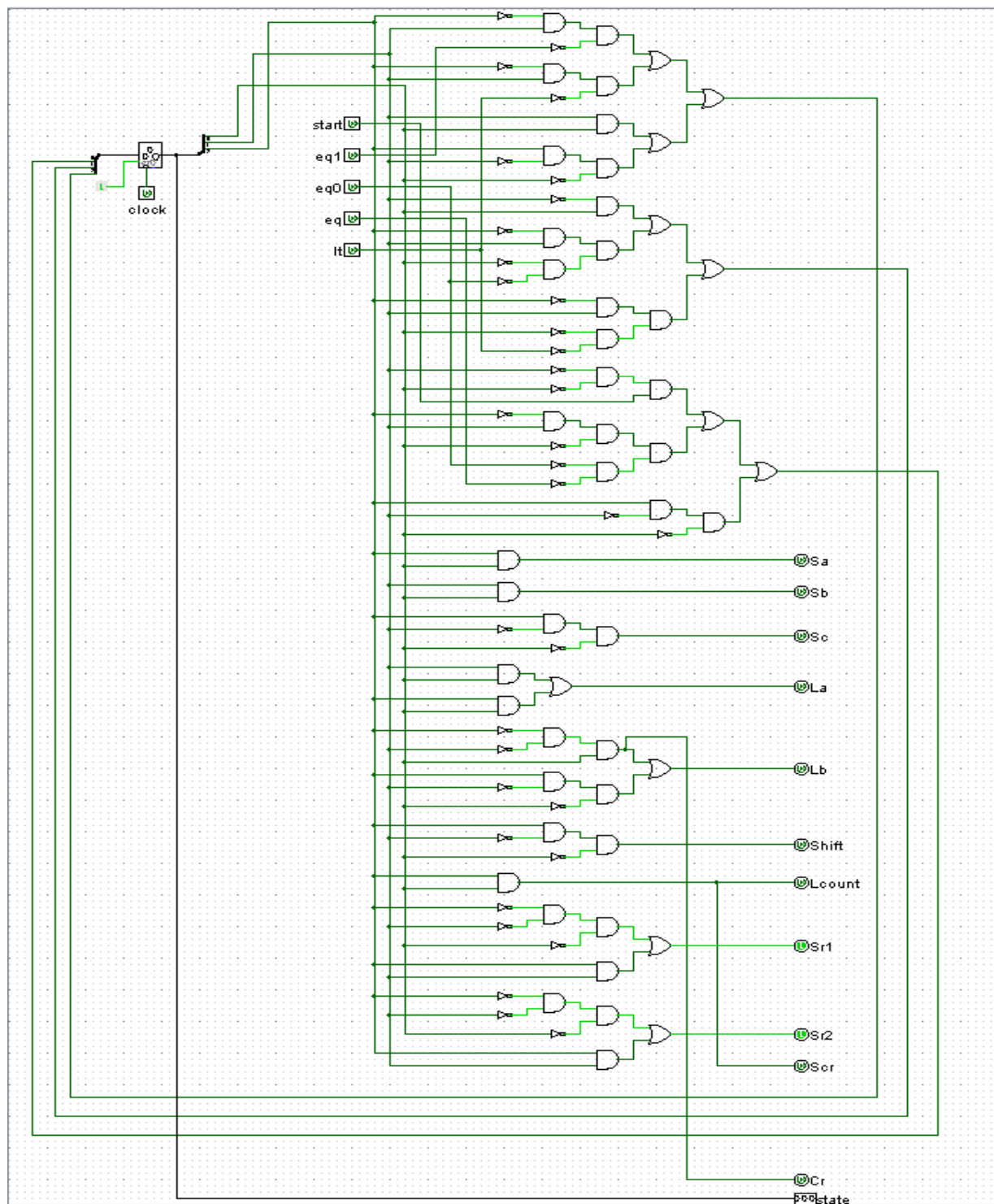
$$N0 = P2'P1'P0'start + P2'P1P0'eq1lt + P2P1'P0'$$




Test Cases

Hi pin holds the most significant 32 bit of result. [63:32]

Lo pin holds the less significant 32 bit of result. [31:0]


Test1

$2 \times 3 = 6$

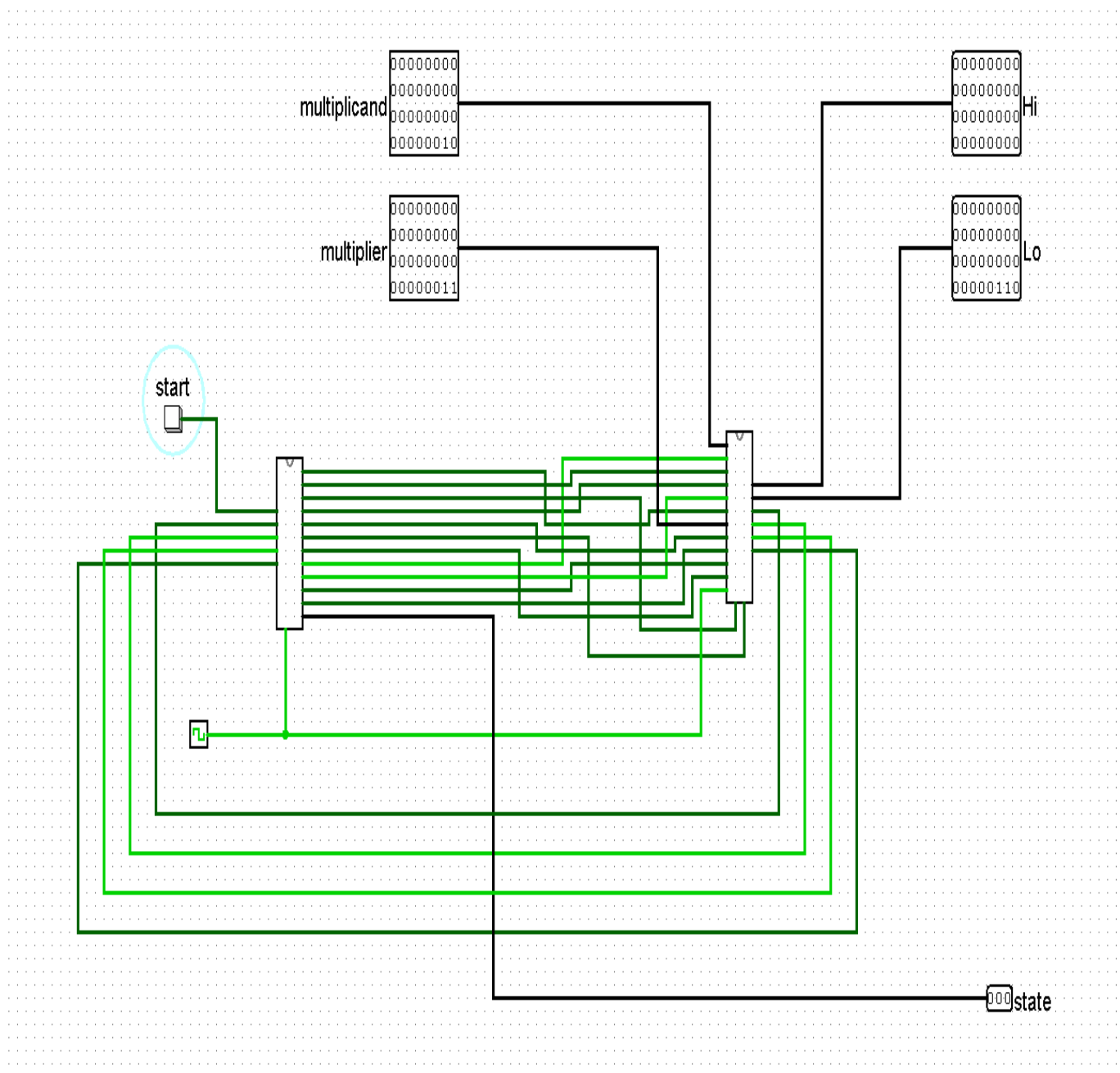


Test 2

$$9 \times 4 = 36$$

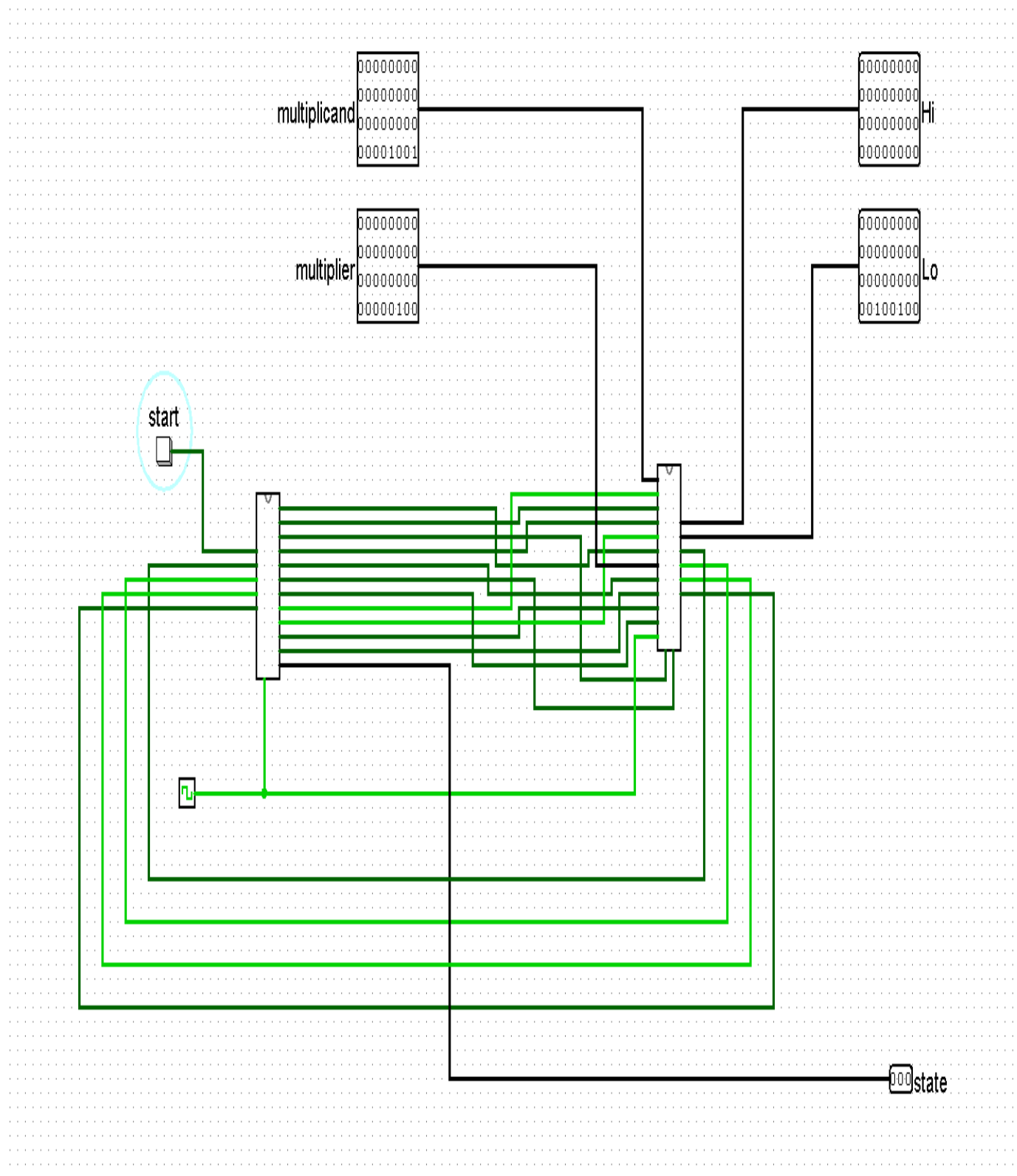


Test 3

$$15 \times 7 = 105$$

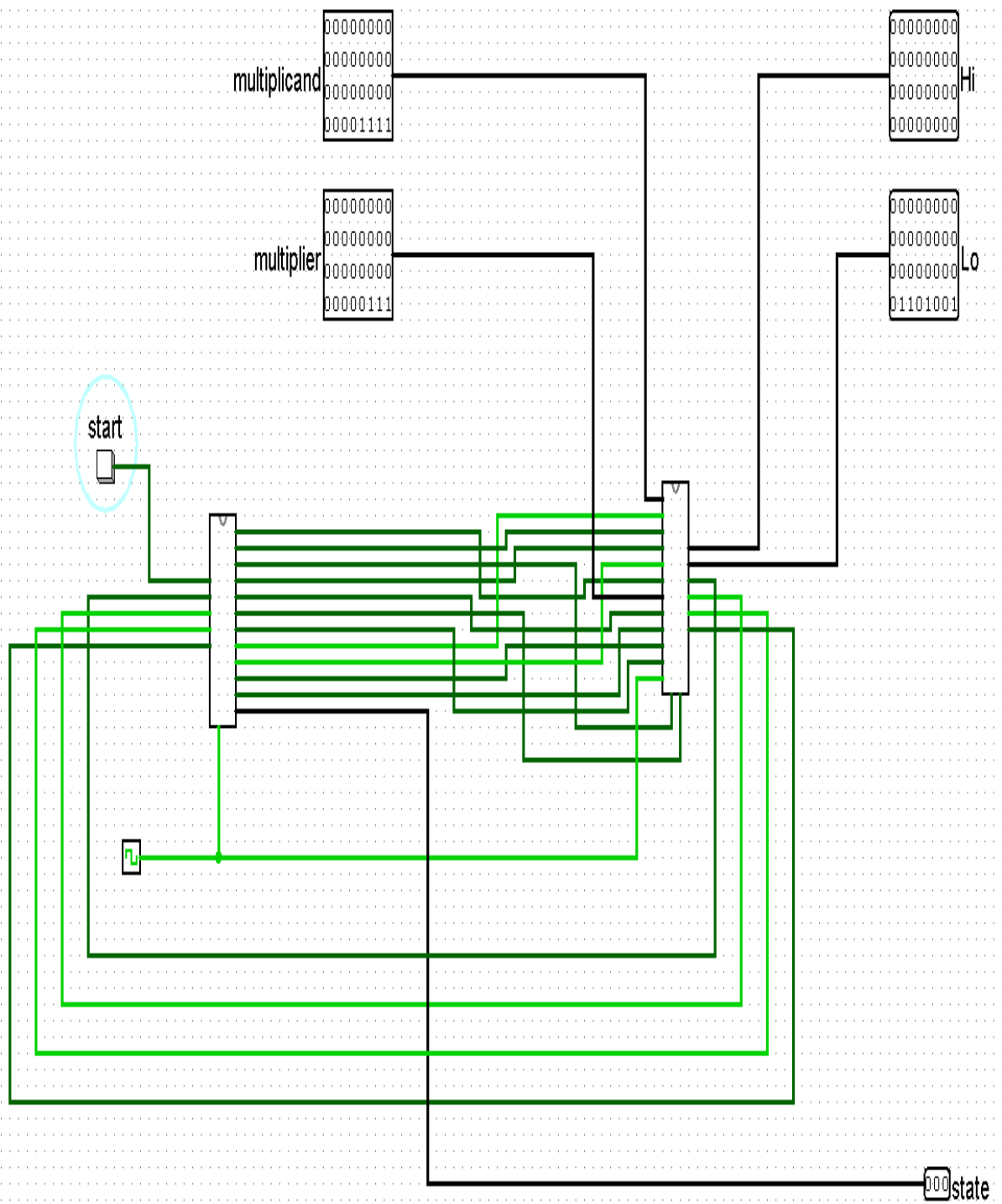


Test 4

$$2^{25} \times 2^{10} = 2^{35}$$

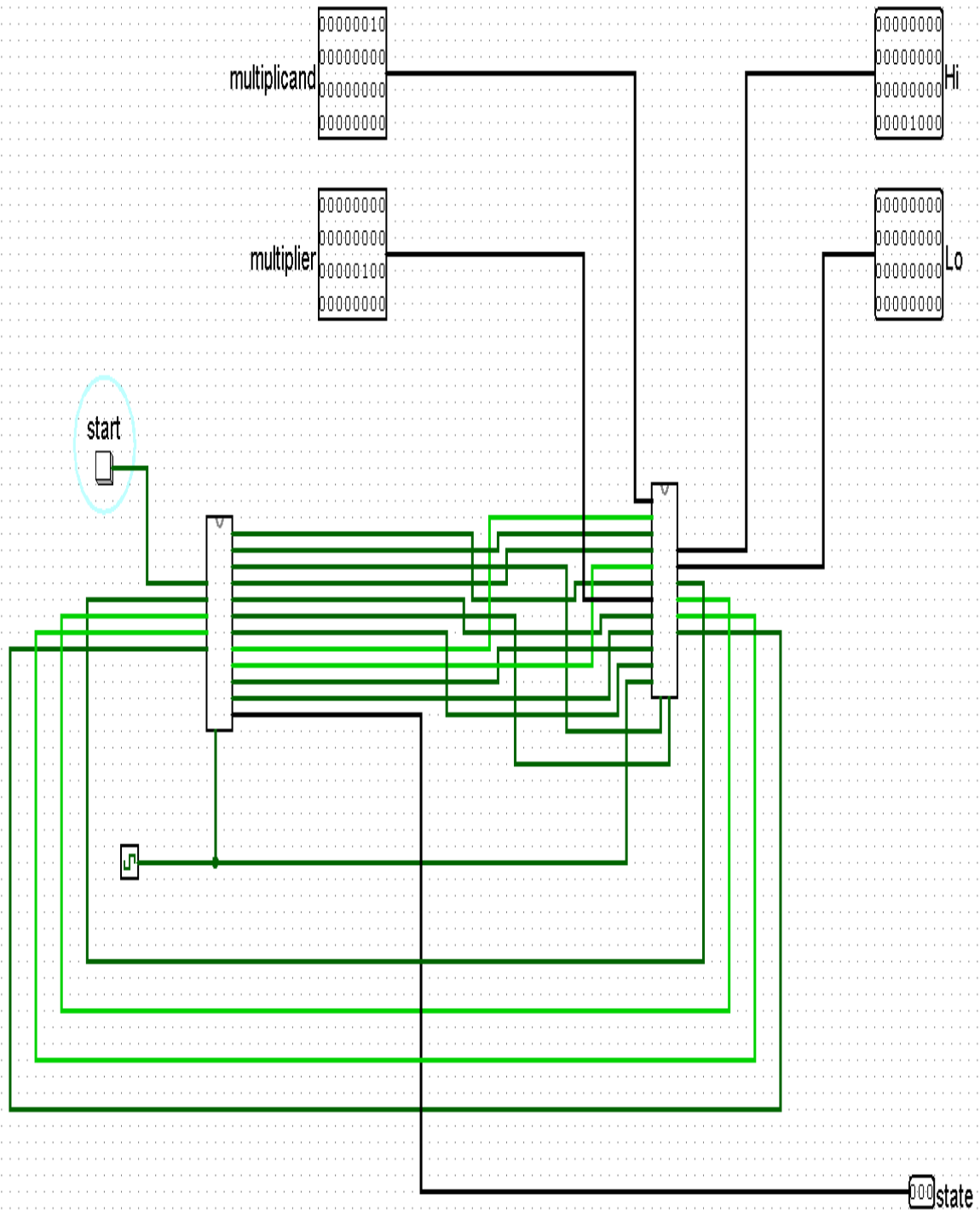


Test 5

$$2^{27} \times 2^{18} = 2^{45}$$

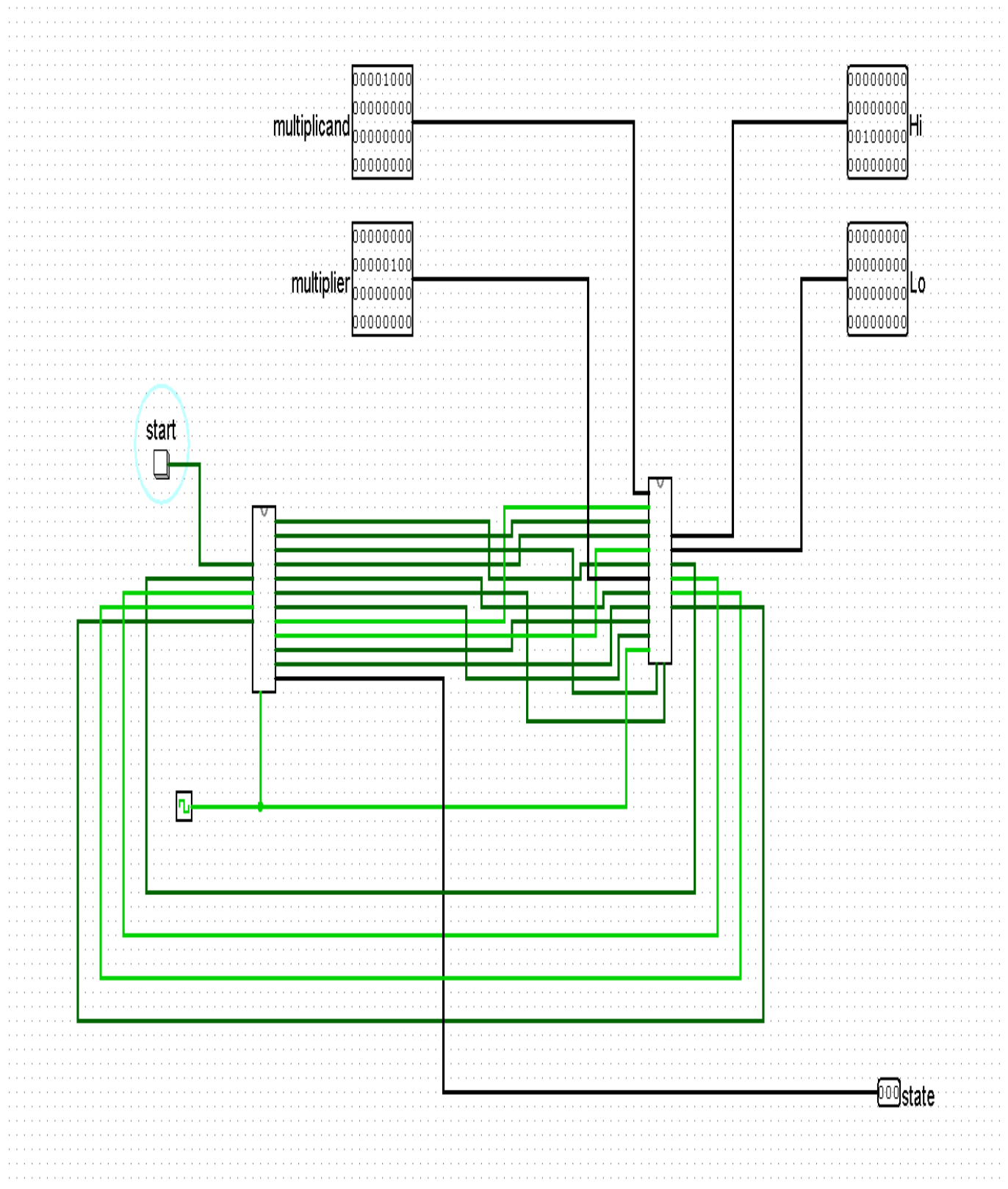

Test 6

$$2^{22} \times 2^{30} = 2^{52}$$

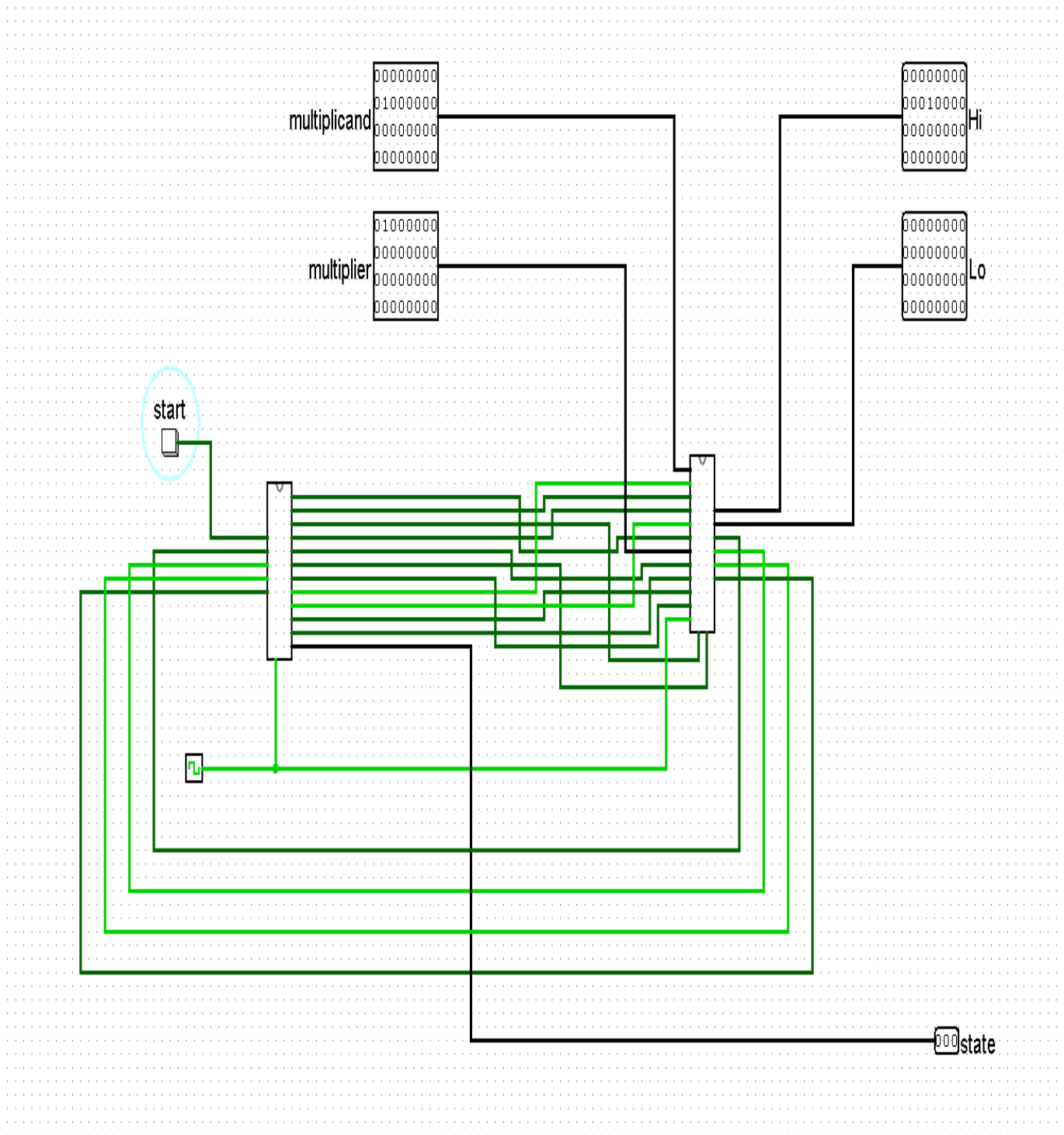

Mehmet Acar

1801042095